

**Al-alamein international university**

**Computer architecture course**


## **ABQM Project**



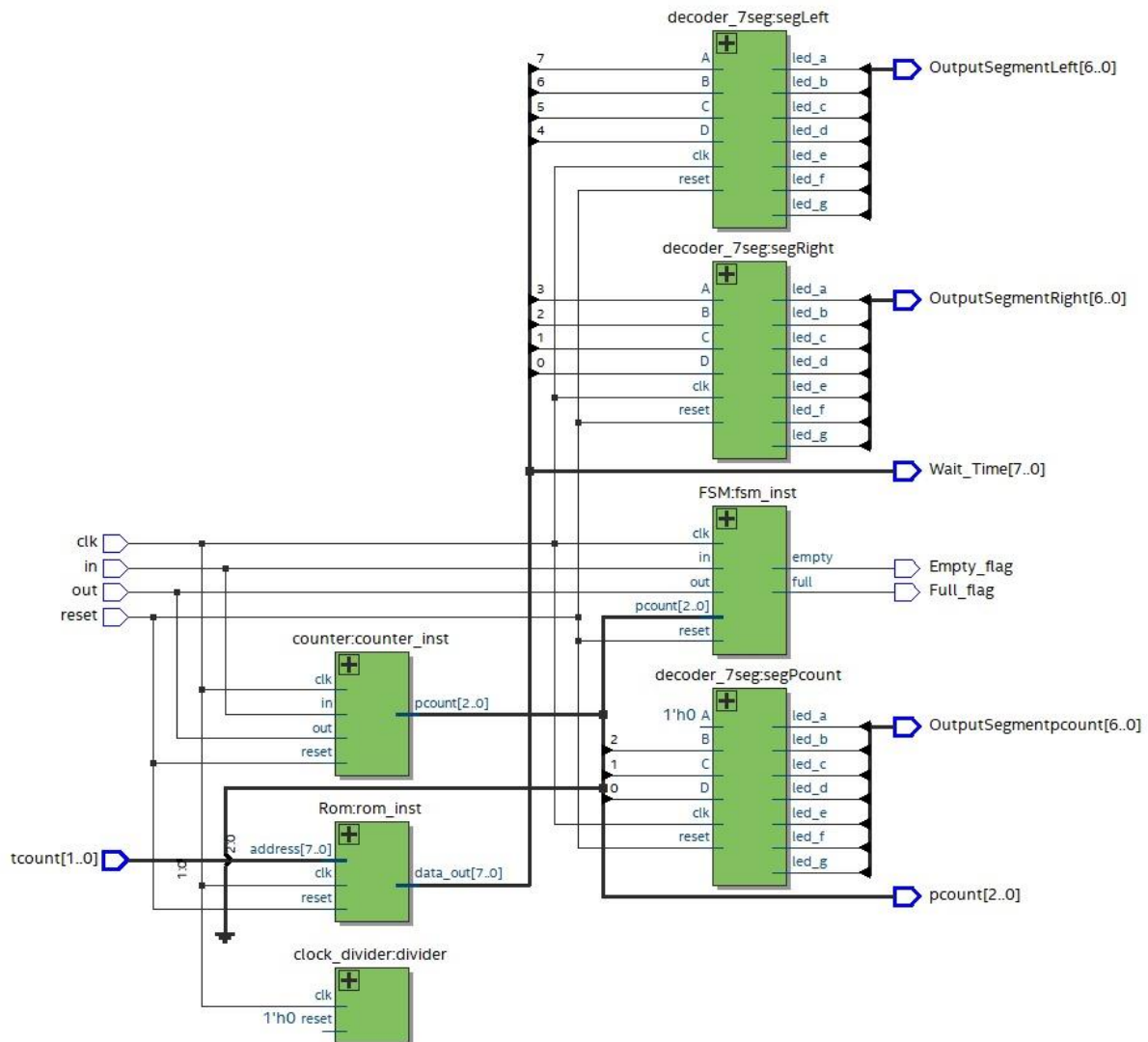
## Project code explanation:


The project consists of 6 modules:

The main module (abqm) . . (Digital clock) module . . (FSM)  
module . . (clock divider) module . . (counter) module . . (Rom)



 

Present State	Next State .....	In .....	Out .....	pcount (value)	Full .....	Empty .....
s0 (Empty)	s1 (Add)	1	0	X	0	0
s0 (Empty)	—	0	0	X	0	1
s1 (Add)	s1 (Add)	1	0	! 3b'111	0	0
s1 (Add)	s2 (Subtract)	0	1	X	0	0
s2 (Subtract)	s0 (Empty)	0	1	3b'000	0	0
s2 (Subtract)	s2 (Subtract)	0	1	! 3b'000	0	0
s2 (Subtract)	s1 (Add)	1	0	X	0	0
s3 (Full)	s2 (Subtract)	0	1	X	0	0
s1(add)	s3(full)	1	0	3b'111	1	0

 

Name	Type and possible values	Description
<b>Reset</b>	Input(0,1)	Reset the system
<b>Clock</b>	Input (0,1)	Timing signal used to ensures that all parts of the system work together in same time
<b>In</b>	Input(0,1)	When some one enter the queue
<b>Out</b>	Input	When some one leave the queue
<b>TCount</b>	Input(1,3)	Number of tillers at the counter
<b>PCount</b>	Output(0,7)	Number of clients at the queue
<b>EmptyFlag,Full flag</b>	Output(0,1)	To indicate that queue is empty or full
<b>7 segmented display Pcount</b>	Output(0,7)	Used to display number of people
<b>7 segmented Display Wtime right</b>	Output(0,7)	Used to display number of waiting time of ones of number
<b>7 segmented Display Wtime left</b>	Output(0,7)	Used to display number of waiting time of tens of number

### Detailed Specifications of ABQM™:

1. Photocells: Both ends of the queue have photocells. Each photocell outputs a logic 1 if the light beam is uninterrupted and switches to logic 0 when the beam is interrupted.
2. Queue Management: Clients enter the queue from the back and leave from the front.
3. Display Information: The number of people in the queue (Pcount) and the expected waiting time (Wtime) are displayed on a Seven Segment Display and empty,full flag.
4. Pcount Adjustment: Pcount increases by one when a client enters the queue and decreases by one when a client leaves, regardless of how long the client stands in front of the photocell.
5. Waiting Time Calculation: Wtime is calculated as follows:
  - If  $Pcount \neq 0$ ,  $Wtime = 3 * (Pcount + Tcount - 1) / Tcount$ , where Tcount (1, 2, or 3) is the number of tellers in service. The fractional part of Wtime is ignored.
6. Status Flags: ABQM™ has binary flags indicating whether the queue is empty or full.
7. System Reset: The system can be reset, by making the full flag is equal to zero . . and Pcount while setting the empty flag to 1.

## FSM module:

### 1. Module Declaration:

- The module has input ports `clk`, `reset`, `in`, and `out`, and output ports `pcount`, `full`, and `empty`.

### 2. State Declaration:

- A register state is declared to store the current state of the FSM.
- The state register is 2 bits wide, indicating that there are four possible states: `s0`, `s1`, `s2`, and `s3`.

### 3. Output Registers:

- Output registers `full` and `empty` are declared to indicate whether the FSM is in a full or empty state, respectively.

### 4. State Definitions:

- State definitions are declared using parameters. Each state is assigned a two-bit binary value.
- `s0` represents the empty state (00), `s1` represents the add state (01), `s2` represents the subtract state (10), and `s3` represents the full state (11).

### 5. always Block:

- The `always` block is sensitive to the positive edge of the clock (`posedge clk`) or the positive edge of the reset signal (`posedge reset`).



- Inside the always block, the behavior of the FSM is defined based on the current state and input signals.

#### 6. Reset Condition:

- If the reset signal is asserted (`reset == 1`), the FSM is reset to the initial state (`state = 0`).
- The empty flag is set to 1 to indicate an empty state, and the full flag is set to 0.

### abqm module:

#### 1. abqm Module:

- Inputs: `clk`, `reset`, `in`, `out`, and `tcount`.
- Outputs: `Full_flag`, `Empty_flag`, `OutputSegmentRight`, `OutputSegmentLeft`, `OutputSegmentpcount`, `Wait_Time`, and `pcount`.
- 

### Digital clock :

The code you provided consists of two modules:

#### 1. decoder\_7seg:

This module is a decoder for a 7-segment LED display. It takes a 4-bit binary input (A, B, C, D) representing a digit and drives

the individual segments (led\_a to led\_g) of the display to show the corresponding number (0-9) or letter (A-F).

- **Inputs:**

- clk (clock): Clock signal for synchronization.
- reset: Active high reset signal to initialize the display.
- A, B, C, D: 4-bit binary input representing the digit or letter to display.

- **Outputs:**

- led\_a to led\_g: Individual outputs that control the segments of the 7-segment display.


The logic uses a series of inverters and AND/OR gates to decode the 4-bit input into the appropriate segment patterns for each digit or letter.

### Counter:

This module implements a counter with a maximum capacity of 7 (represented by a 3-bit register pcount). It takes the following signals:

- **clk (clock):** A clock signal that triggers the counter's operation on its positive edge.
- **reset (active high):** A reset signal that initializes the counter to 0 (3'b000) when asserted.
- **in:** An input signal that controls incrementing the counter.
- **out:** An input signal that controls decrementing the counter.

The counter has a single output:

 

- **pcount (output reg [2:0]):** A 3-bit register that stores the current count value (0 to 7).

Here's how the code functions:

1. **Always Block:** The entire logic resides within an `always` block that executes on every positive edge of the clock (`posedge clk`) or when the reset signal is asserted (`posedge reset`).
2. **Reset:** If the reset signal is active (high), the `pcount` register is set to 0 (`3'b000`), effectively resetting the counter.
3. **Increment:** If the `in` signal is active (high) and the current count (`pcount`) is less than the maximum value (`3'b111`), the counter increments by 1. This ensures the counter doesn't overflow beyond its capacity.
4. **Decrement:** If the `out` signal is active (high) and the current count (`pcount`) is greater than the minimum value (`3'b000`), the counter decrements by 1. This prevents the counter from underflowing below 0.

## Rom:

This module called Rom. This module acts as a Read-Only Memory (ROM). Here's a breakdown of its functionality:

### Inputs:

- **clk (clock):** A clock signal that triggers the ROM operation on its positive edge.
- **reset (active high):** A reset signal that initializes the ROM's output to 0 (all bits set to 0) when asserted.
- **address (input [7:0]):** An 8-bit address that specifies the location of the data to be read from the ROM.

### Output:

- **data\_out (output reg [7:0]):** An 8-bit register that stores the data read from the ROM based on the provided address.

### Functionality:

1. **Always Block:** The logic resides within an `always` block that executes on every positive edge of the clock (`posedge clk`) or when the reset signal is asserted (`posedge reset`).
2. **Reset:** If the reset signal is active (high), the `data_out` register is set to 0 (`8'b00000000`), effectively clearing the output.

### **Team members:**

Youssif Yasser said	22100809
Mohammed ahmed shoukry	22100259
Mahmoud eid Khamis	22100680